



ANALOG CIRCUIT DESIGN

DISCRETE AND INTEGRATED

Sergio Franco

San Francisco State University

**Mc
Graw
Hill**
Education



ANALOG CIRCUIT DESIGN: DISCRETE AND INTEGRATED

Published by McGraw-Hill Education, 2 Penn Plaza, New York, NY 10121. Copyright © 2015 by McGraw-Hill Education. All rights reserved. Printed in the United States of America. No part of this publication may be reproduced or distributed in any form or by any means, or stored in a database or retrieval system, without the prior written consent of McGraw-Hill Education, including, but not limited to, in any network or other electronic storage or transmission, or broadcast for distance learning.

Some ancillaries, including electronic and print components, may not be available to customers outside the United States.

This book is printed on acid-free paper.

1 2 3 4 5 6 7 8 9 0 DOC/DOC 1 0 9 8 7 6 5 4

ISBN 978-0-07-802819-9

MHID 0-07-802819-1

Senior Vice President, Products & Markets: *Kurt L. Strand*

Vice President, General Manager: *Marty Lange*

Vice President, Content Production & Technology Services: *Kimberly Meriwether David*

Global Publisher: *Raghu Srinivasan*

Marketing Manager: *Nick McFadden*

Director, Content Production: *Terri Schiesl*

Lead Project Manager: *Jane Mohr*

Buyer: *Laura Fuller*

Cover Designer: *Studio Montage, St. Louis, MO*

Cover Image: © *Brand X/Superstock*

Compositor: *MPS Limited*

Typeface: *10/12 Times*

Printer: *R. R. Donnelley*

All credits appearing on page or at the end of the book are considered to be an extension of the copyright page.

Library of Congress Cataloging-in-Publication Data

Franco, Sergio.

Analog circuit design : discrete and integrated / Sergio Franco, professor of EECS at San Francisco State University.

pages cm

Includes bibliographical references and index.

ISBN 978-0-07-802819-9 (alk. paper)

I. Electronic circuit design. I. Title.

TK7867.F687 2015

621.3815—dc23

2013035489

The Internet addresses listed in the text were accurate at the time of publication. The inclusion of a website does not indicate an endorsement by the authors or McGraw-Hill Education, and McGraw-Hill Education does not guarantee the accuracy of the information presented at these sites.

Contents

Preface ix

Chapter 1

Diodes and the *pn* Junction 1

- 1.1 The Ideal Diode 3
- 1.2 Basic Diode Applications 10
- 1.3 Operational Amplifiers and Diode Applications 21
- 1.4 Semiconductors 25
- 1.5 The *pn* Junction in Equilibrium 34
- 1.6 Effect of External Bias on the SCL Parameters 39
- 1.7 The *pn* Diode Equation 43
- 1.8 The Reverse-Biased *pn* Junction 50
- 1.9 Forward-Biased Diode Characteristics 53
- 1.10 Dc Analysis of *pn* Diode Circuits 58
- 1.11 Ac Analysis of *pn* Diode Circuits 67
- 1.12 Breakdown-Region Operation 76
- 1.13 Dc Power Supplies 84
 - Appendix 1A: SPICE Models for Diodes 90
 - References 93
 - Problems 93

Chapter 2

Bipolar Junction Transistors 109

- 2.1 Physical Structure of the BJT 112
- 2.2 Basic BJT Operation 117
- 2.3 The *i-v* Characteristics of BJTs 130
- 2.4 Operating Regions and BJT Models 137
- 2.5 The BJT as an Amplifier/Switch 150
- 2.6 Small-Signal Operation of the BJT 157
- 2.7 BJT Biasing for Amplifier Design 169
- 2.8 Basic Bipolar Voltage Amplifiers 177

- 2.9 Bipolar Voltage and Current Buffers 189
 - Appendix 2A: SPICE Models for BJTs 201
 - References 203
 - Problems 203

Chapter 3

MOS Field-Effect Transistors 221

- 3.1 Physical Structure of the MOSFET 224
- 3.2 The Threshold Voltage V_t 226
- 3.3 The *n*-Channel Characteristic 237
- 3.4 The *i-v* Characteristics of MOSFETs 247
- 3.5 MOSFETs in Resistive Dc Circuits 259
- 3.6 The MOSFET as an Amplifier/Switch 273
- 3.7 Small-Signal Operation of the MOSFET 282
- 3.8 Basic MOSFET Voltage Amplifiers 290
- 3.9 MOSFET Voltage and Current Buffers 300
- 3.10 The CMOS Inverter/Amplifier 306
 - Appendix 3A: SPICE Models for MOSFETs 314
 - References 316
 - Problems 316

Chapter 4

Building Blocks for Analog Integrated Circuits 332

- 4.1 Design Considerations in Monolithic Circuits 334
- 4.2 BJT Characteristics and Models Revisited 342
- 4.3 MOSFET Characteristics and Models Revisited 357
- 4.4 Darlington, Cascode, and Cascade Configurations 371
- 4.5 Differential Pairs 386

- 4.6 Common-Mode Rejection Ratio in Differential Pairs 396
- 4.7 Input Offset Voltage/Current in Differential Pairs 404
- 4.8 Current Mirrors 409
- 4.9 Differential Pairs with Active Loads 421
- 4.10 Bipolar Output Stages 432
- 4.11 CMOS Output Stages 440
 - Appendix 4A: Editing SPICE Netlists 445
 - References 446
 - Problems 446

Chapter 5

Analog Integrated Circuits 472

- 5.1 The μ A741 Operational Amplifier 473
- 5.2 The Two-Stage CMOS Operational Amplifier 487
- 5.3 The Folded-Cascode CMOS Operational Amplifier 495
- 5.4 Voltage Comparators 501
- 5.5 Current and Voltage References 510
- 5.6 Current-Mode Integrated Circuits 521
- 5.7 Fully Differential Operational Amplifiers 532
- 5.8 Switched-Capacitor Circuits 541
 - Appendix 5A: SPICE Macro-Models 553
 - References 554
 - Problems 554

Chapter 6

Frequency and Time Responses 564

- 6.1 High-Frequency BJT Model 566
- 6.2 High-Frequency MOSFET Model 574
- 6.3 Frequency Response of CE/CS Amplifiers 581
- 6.4 Frequency Response of Differential Amplifiers 592
- 6.5 Bipolar Voltage and Current Buffers 599

- 6.6 MOS Voltage and Current Buffers 606
- 6.7 Open-Circuit Time-Constant (OCTC) Analysis 612
- 6.8 Frequency Response of Cascode Amplifiers 623
- 6.9 Frequency and Transient Responses of Op Amps 629
- 6.10 Diode Switching Transients 639
- 6.11 BJT Switching Transients 644
- 6.12 Transient Response of CMOS Gates and Voltage Comparators 652
 - Appendix 6A: Transfer Functions and Bode Plots 665
 - References 672
 - Problems 672

Chapter 7

Feedback, Stability, and Noise 685

- 7.1 Negative-Feedback Basics 688
- 7.2 Effect of Feedback on Distortion, Noise, and Bandwidth 695
- 7.3 Feedback Topologies and Closed-Loop I/O Resistances 704
- 7.4 Practical Configurations and the Effect of Loading 714
- 7.5 Return Ratio Analysis 741
- 7.6 Blackman's Impedance Formula and Injection Methods 755
- 7.7 Stability in Negative-Feedback Circuits 762
- 7.8 Dominant-Pole Compensation 772
- 7.9 Frequency Compensation of Monolithic Op Amps 780
- 7.10 Noise 795
 - References 811
 - Problems 811

Index 827